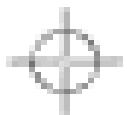


# Circuits De-mystified:

## Measuring Impedance

Question:

- How do you work out the (source) impedance of a circuit (at a given point)?





# Circuits De-mystified:
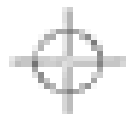
## Measuring Impedance

Answer:


- You do not need need a whole lot of complicated maths!
- You can use some basic circuit principles instead




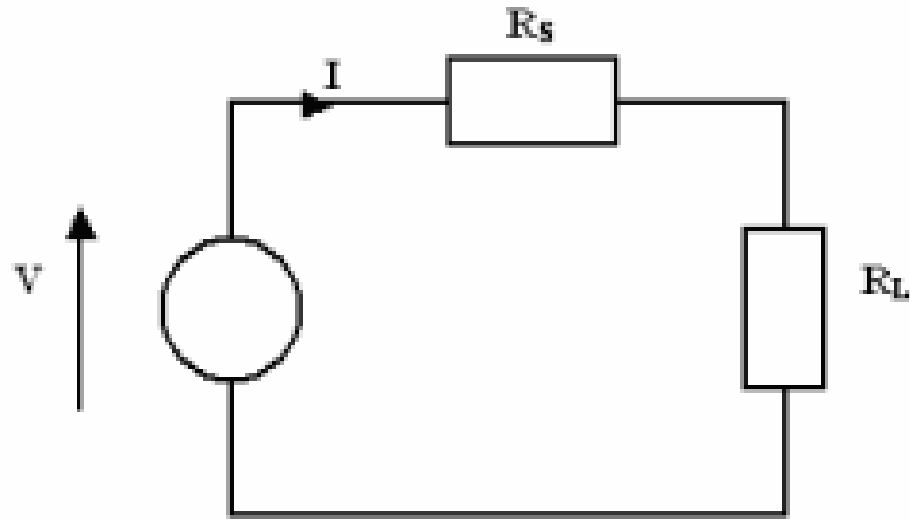


Source: <https://commons.wikimedia.org/wiki/File:Maxpowertheorem.png>  
Source: [https://en.wikipedia.org/wiki/Maximum\\_power\\_transfer\\_theorem](https://en.wikipedia.org/wiki/Maximum_power_transfer_theorem)

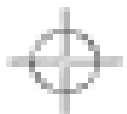
- In every “source”, we have an ideal voltage,  $V$ , and some Source Resistance,  $R_S$
- 'looks like the “model” of the internal resistance of a battery – it's the same idea really



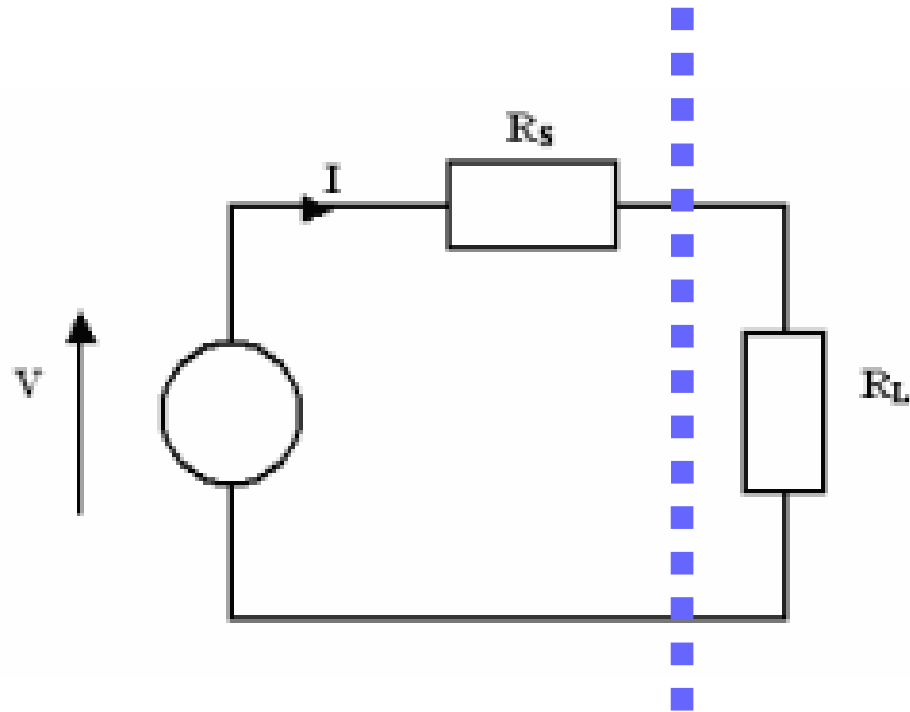


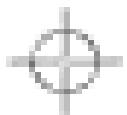
- The load resistance is  $R_L$
- *(In an alternating current circuit,  $Z=R+Xj$ , we will look at this later...)*



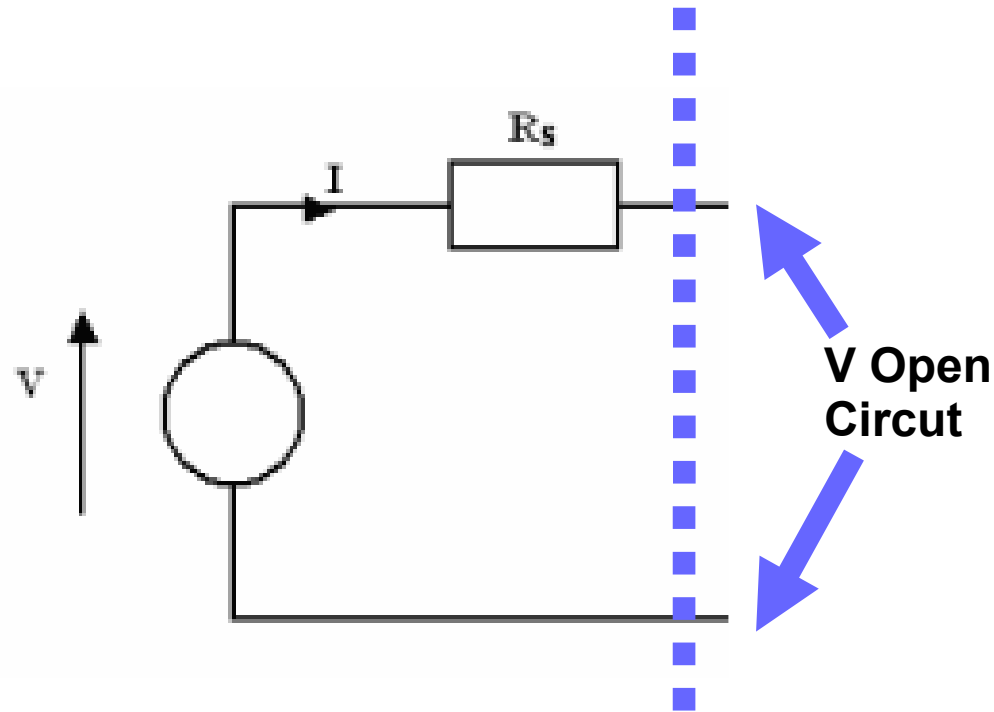


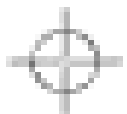
- If the circuit has no load, “Open circuit voltage” will be the same as the perfect source voltage



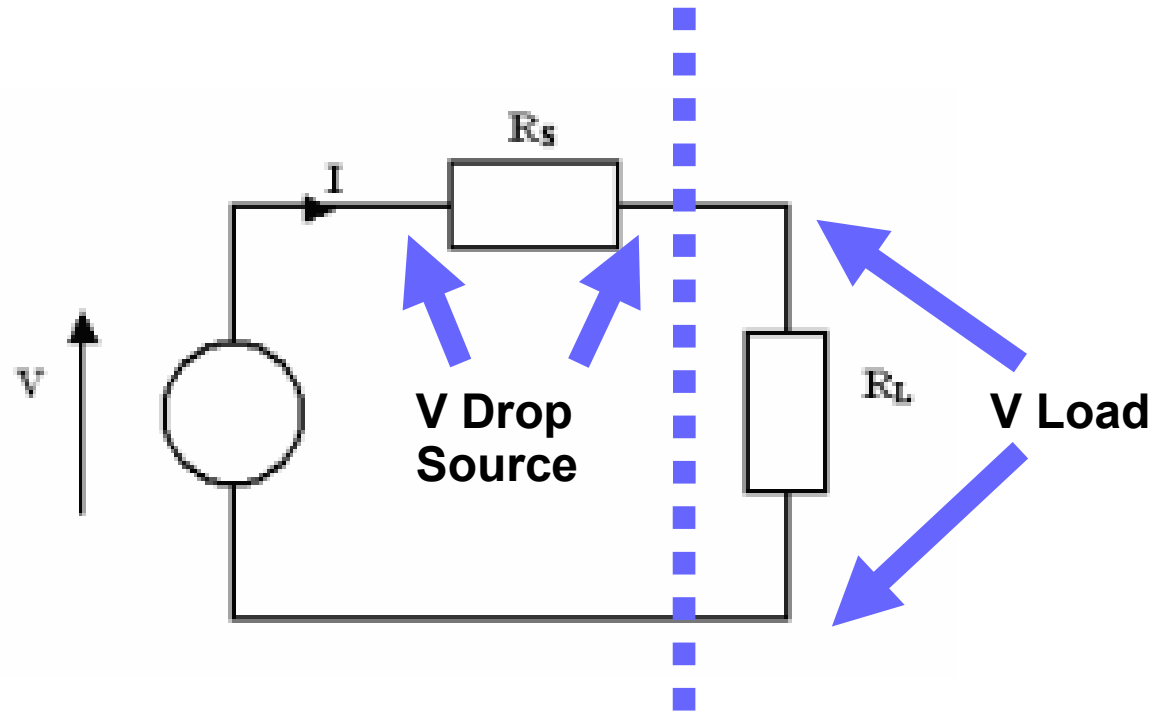


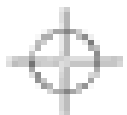
- As load increases, from Ohm's law, voltage will “drop” across the internal resistance,  $R_S$



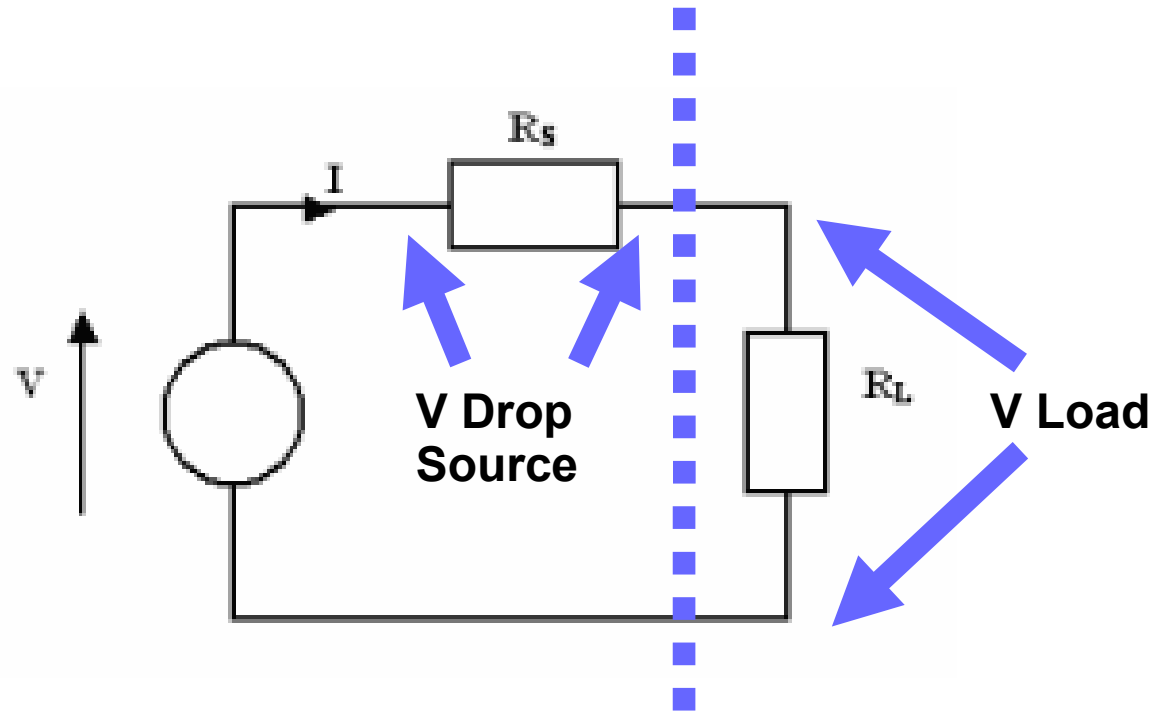


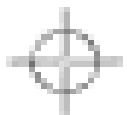- By inspection, if  $R_L = R_S$ , then the voltage across both will be equal
- **This means the load voltage will be half the voltage of the Open Source voltage**




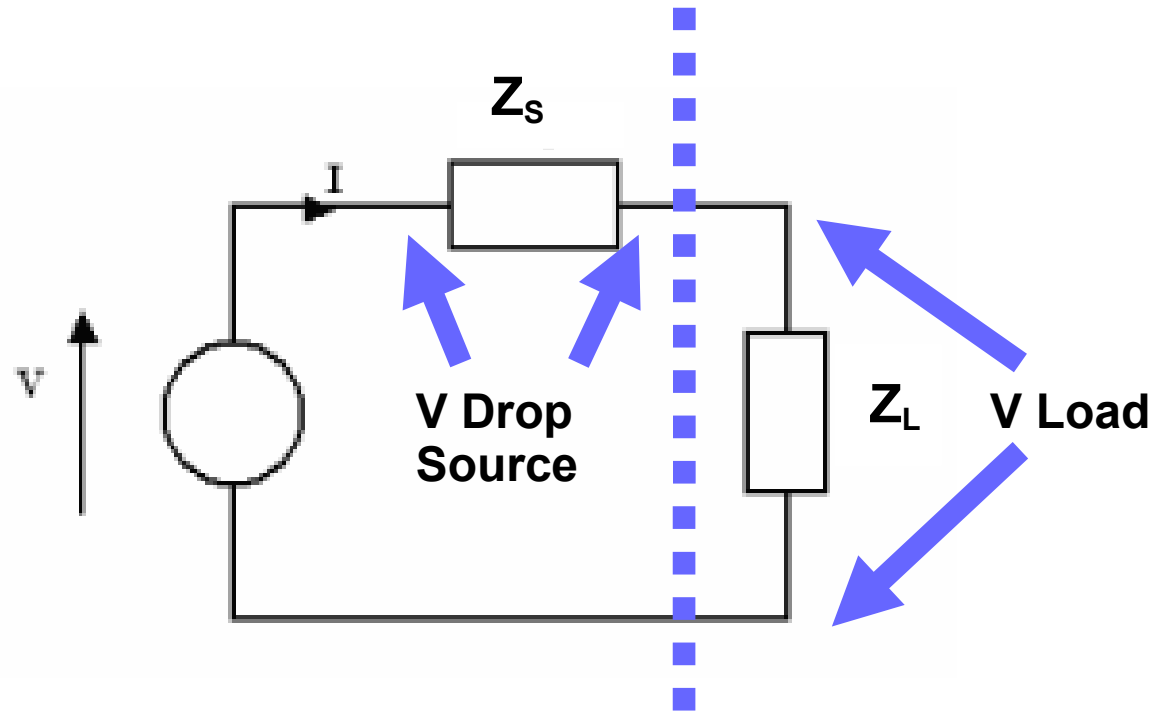

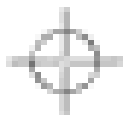
- It can be shown for an a.c. circuit, the same principle applies for Impedance
- When  $Z_L = Z_S$  , then the voltage across both impedances will be equal






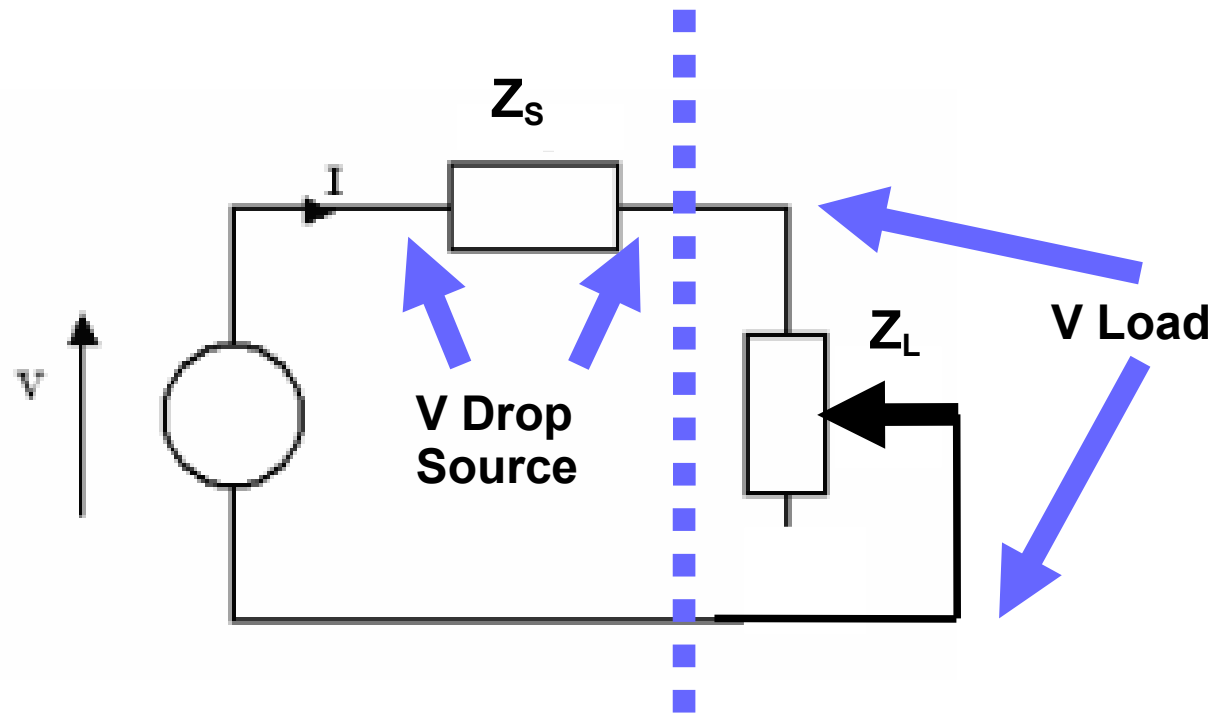

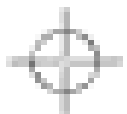
- Using the voltage halving idea, we can apply a variable load to see the change this makes to the (load) voltage in the circuit
- When  $V_{\text{Load}} = (1/2) * V_{\text{Open Circuit}}$ , then  $Z_L = Z_s$



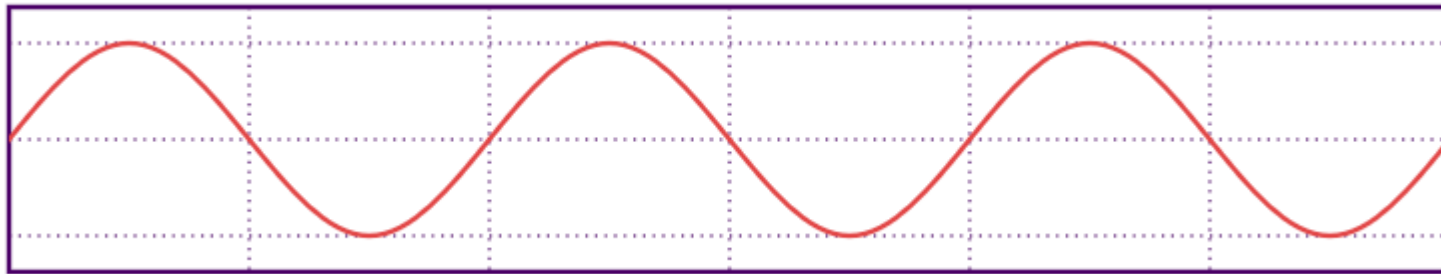


V Open  
Circuit

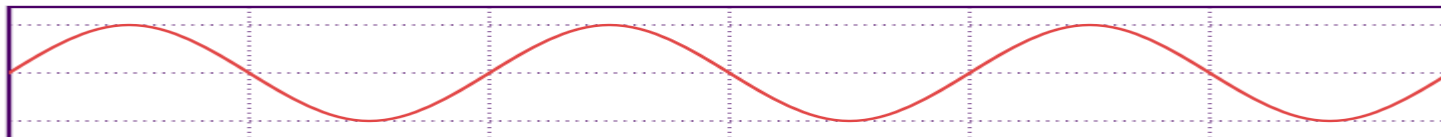
Source: [https://en.wikipedia.org/wiki/Sine\\_wave#/media/File:Waveforms.svg](https://en.wikipedia.org/wiki/Sine_wave#/media/File:Waveforms.svg)  
 Source: [https://en.wikipedia.org/wiki/Sine\\_wave](https://en.wikipedia.org/wiki/Sine_wave)




V Load

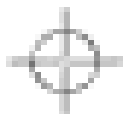- When  $V_{Load} = (1/2) * V_{Open\ Circuit}$ , then  $Z_L = Z_S$
- There is a video from W2AEW, Alan, that shows this in action: <https://www.youtube.com/watch?v=ieAhBejHe2M>



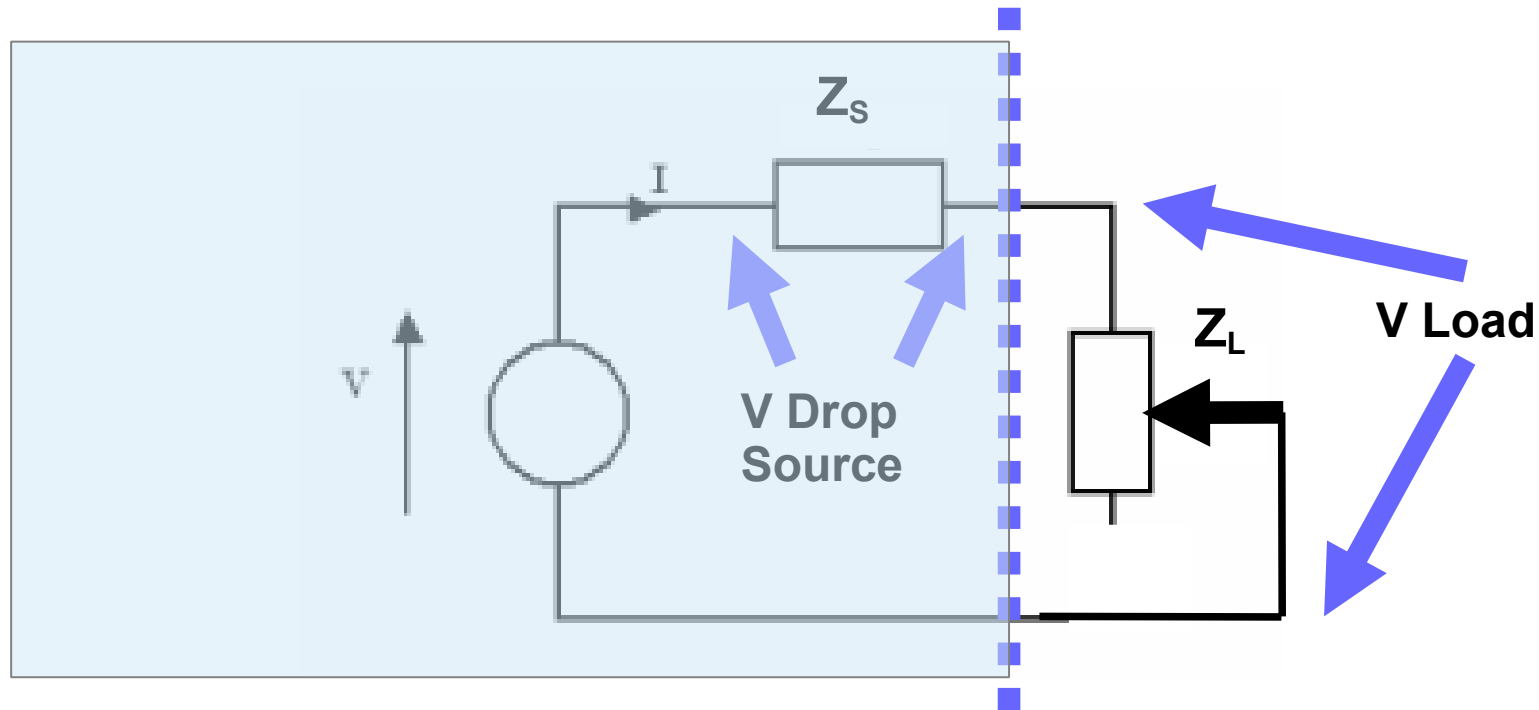


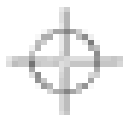- In principle this idea could be applied to any given point in a circuit, so you would have a technique to measure impedance for different parts of the circuit – provided there is a source voltage to measure



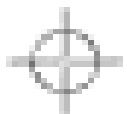
## *Practicalities and challenges!*

- Not all circuits work with this technique or are easily measurable at RF frequencies (due to reflection), as Alan W2AEW describes
- Some circuits prefer a high impedance load only or behave strangely depending on load or measure better if the source is “smooth” like a sine wave or constant voltage
- 'a circuit loaded to a point it's voltage halves... though it may not be able to dissipate that much power or have been designed to do that




# The in-depth method?

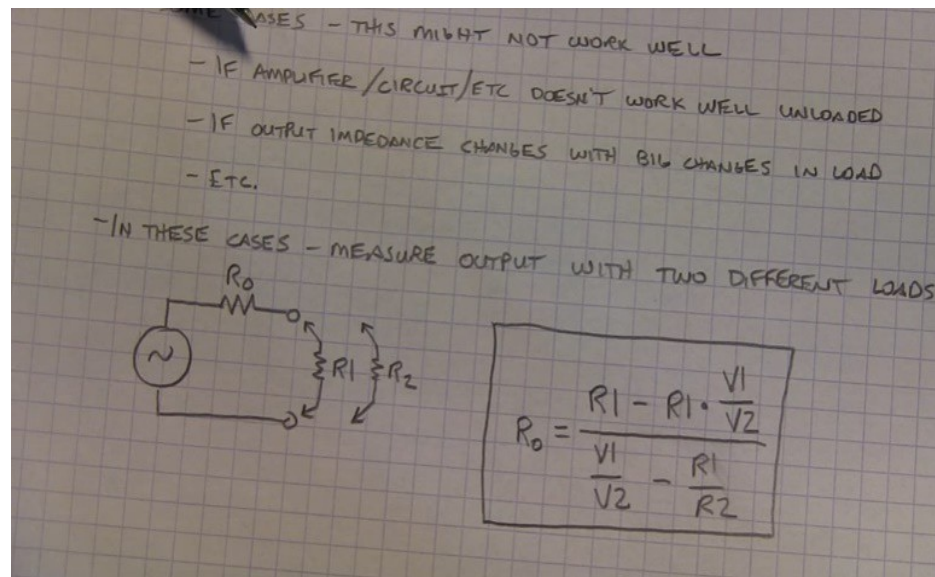


Source: <https://www.youtube.com/watch?v=ieAhBejHe2M>

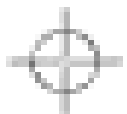- You can measure voltage of the circuit for two “normal” loading points and infer impedance from this
- Could be more suitable in some cases



***Any questions?***

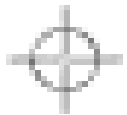

TARGet Nite

